

AHSANULLAH UNIVERSITY OF SCIENCE & TECHNOLOGY

COURSE NO : 2211

COURSE TITLE : measurement & Instrumentation

PROJECT : MAZE SOLVER

submitted by

Tazmir Hamid - 11.02.05.078

Shahab Moji - 11.02.05.082

Pritom chowdhury - 11.02.05.091

Faham Ahmed Khan - 11.02.05.101



Objective :

~~The~~ The objective of this experiment is to build a maze-solving Robot without micro-controller.

Equipments:

- 1) BJT (BD681) 2 Pcs
- 2) POT (10K) Pcs
- 3) LDR 6 Pcs
- 4) LED 11 Pcs
- 6) Resistance 1K-2 Pcs, 220 Ω -2 Pcs
- 7) DC motor with wheel - 2 Pcs
- 8) connecting wires
- 9) bread board
- 10) Diode - 2 Pcs
- 11) DC Adapter - 1

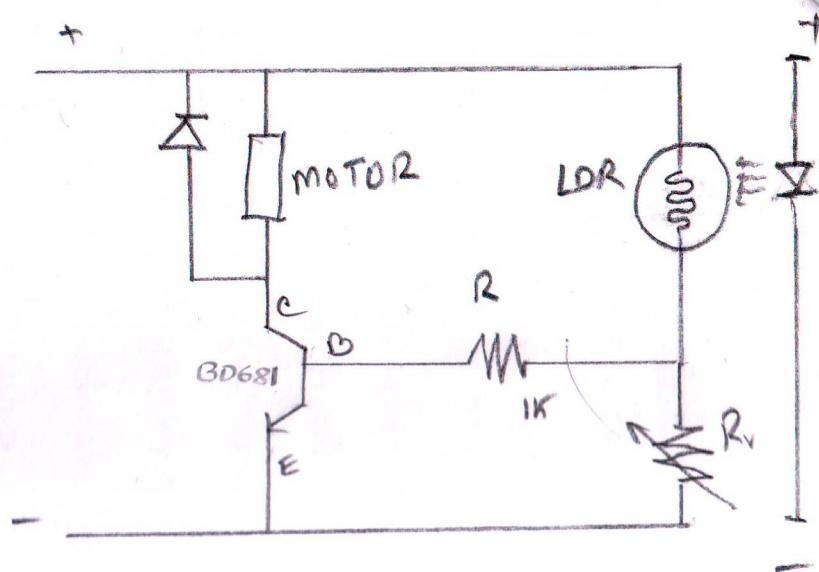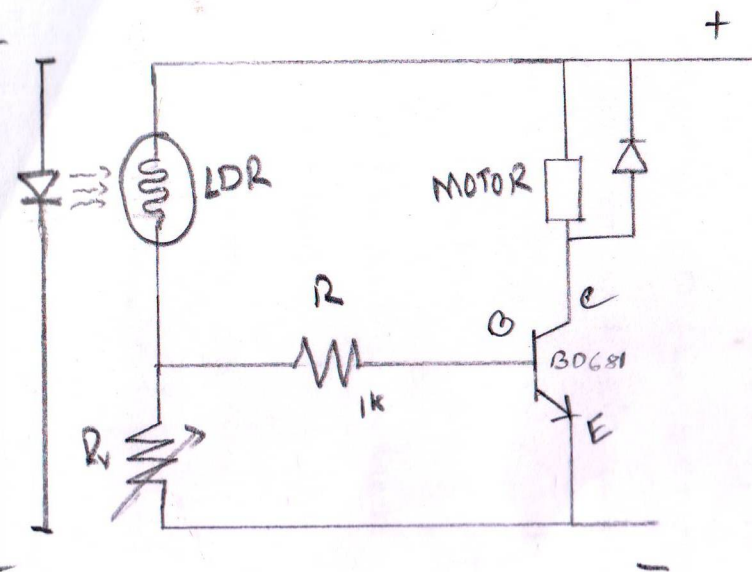11.02.05.78
11.02.05.82
11.02.05.91
11.02.05.101



11.02.05.7
11.02.05.7
11.02.05.7

Working Principal:

We are using BJT, LDR, Pot and resistance, motor Diode. We are using BJT as a switch. We need to close the switch for closing the switch, we need voltage across the BE terminal (across the Pot). When the voltage is applied the LDR takes all voltage because the LDR resistance is too high when the LDR isn't getting any light. When the LDR is getting light which is reflecting from the wall, then the resistance of LDR is low so the voltage drop is happening across the BE terminal, so the BJT is conducting current so the motor turns. We are using $1K$ resistance for safety in B terminals because the input impedance is low. We are using Diode because after turning the motor, when the BJT is off again, then the motor will not stop right the moment. So it will work as a generator according to DC Motor principle, so the generated voltage couldn't do any harm at circuit. Actually in circuit is for following two wall. It can solve and solve $\perp$ shape maze. It can't solve T shape maze because when the robot is in T shape maze the two motors will stop as the circuit designed.

It's the limitation of this Robot.

TROUBLE SHOOTING

Qus: Where should we place the LDR?

Ans:

We should place the LDR behind the front wheel and the LDR must be in Parallel with the center of the wheel.

Qus: Which kind of supply should we use?

Ans:

We can use DC Battery and DC Adapter as a source. But there are some problem in using Battery. If the current rating of the Battery is not high then it will not work properly. So, working with DC adapter is suitable.

Qus: Which kind of LED should we use?

Ans: We have use Brighter LED. Otherwise we couldn't get proper Reflection.

Qus: How LDR Responds?

Ans: As a sensor LDR is not very good. It has a very poor sensitivity. That's why we used three LDR in Parallel.

Qus: Which kind of BJT should we use?

Ans: In this Project we use High gain BJT. We could also use low gain BJT. But there will be some problem. If high amount of current go through that BJT. it will be damaged. That's why we use high gain BJT.

Qus: Why we use a resistance along with BJT?

Ans: In this ckt the input impedance is very low that's why we use, a $1k\Omega$ Resistance with Base terminal.

Qus: How much voltage we should apply?

Ans: supply voltage should be between $10-12V$

Qus: Where should we construct the circuit?

Ans: we can construct the ckt in Vero board and also in bread board. Both have some limitations. In vero board some time ckt may not work properly. In bread board connection can be disconnected from the board.

11.02.05.78
11.02.05.82
11.02.05.91
11.02.05.101