

Battery Monitoring Device

Submitted by :

11.01.05.072

11.01.05.077

11.01.05.080

11.01.05.084

11.01.05.104

Equipment:

1. LM3914-N IC

2. 100k & 50k pot

3. Resistor- 100k, 5.1k

4. Capacitor 4700uf

5. 50 LEDs lights

6. Bread-board

7. Wire

8. Variable DC supply

Features of LM 3914:

1. Drives LEDs, LCDs or vacuum fluorescent

11.01.05.072
11.01.05.077
11.01.05.080
11.01.05.084
11.01.05.104

Objective:

The objective of this project is to monitor the charge of a battery. We can easily change division of monitoring and range.

Equipment:

1. LM3914-N IC
2. 100k & 50 k pot
3. Resistor- 100k, 5.1k
4. Capacitor 4700uF
5. 10 LED lights
6. Bread board
7. Wire
8. Variable DC supply

Features of LM 3914:


1. Drives LEDs, LCDs or vacuum fluorescents

10.01.05.072
10.01.05.077
10.01.05.080
10.01.05.084
10.01.05.104

2. Bar or dot display mode externally selectable by user
3. Expandable to displays of 100 steps
4. Internal voltage reference from 1.2V to 12V
5. Operates with single supply of less than 3V
6. Inputs operate down to ground
7. Output current programmable from 2 mA to 30 mA
8. No multiplex switching or interaction between outputs
9. Input withstands $\pm 35\text{V}$ without damage or false outputs
10. LED driver outputs are current regulated, open-collectors
11. Outputs can interface with TTL or CMOS logic
12. The internal 10-step divider is floating and can be referenced to a wide range of voltages

Circuit Diagram (by Proteus):

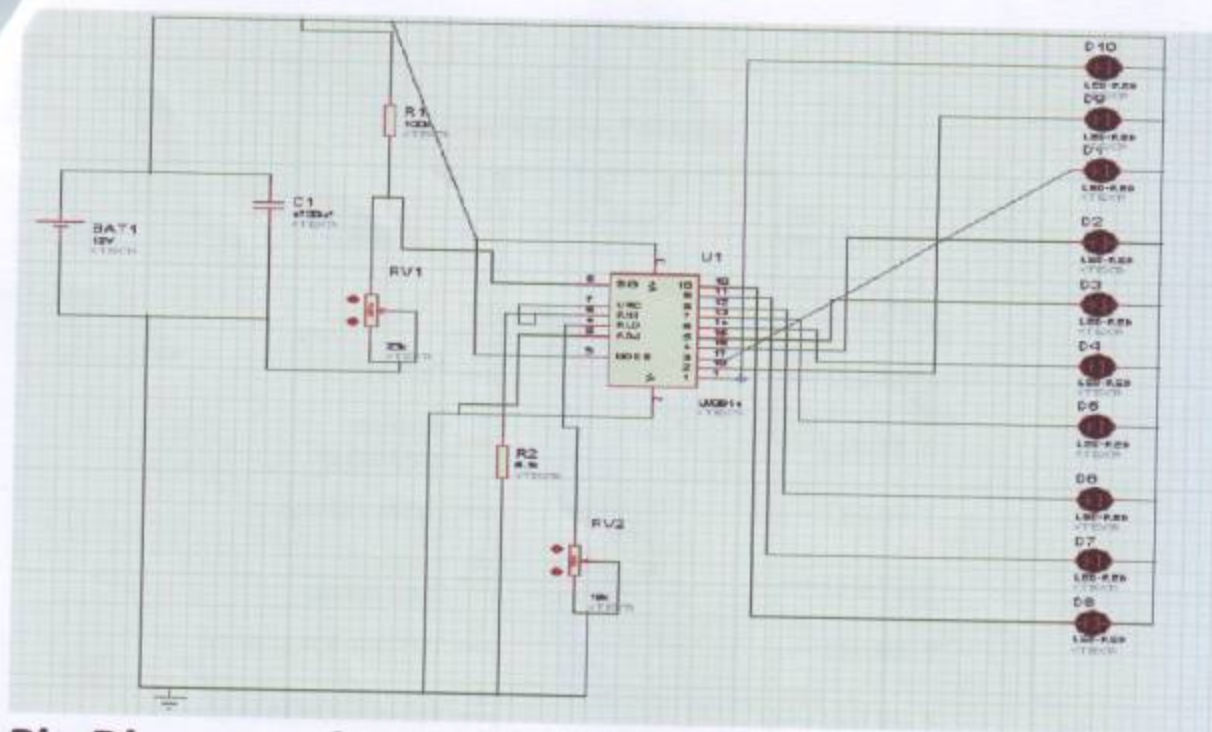10.01.05.072
10.01.05.077
10.01.05.080
10.01.05.084
10.01.05.104




Pin Diagram of LM3914-N:

Back Bar Graph Meter:

10.01.05.072
10.01.05.077
10.01.05.080
10.01.05.084
10.01.05.104

Dual-in-Line Package

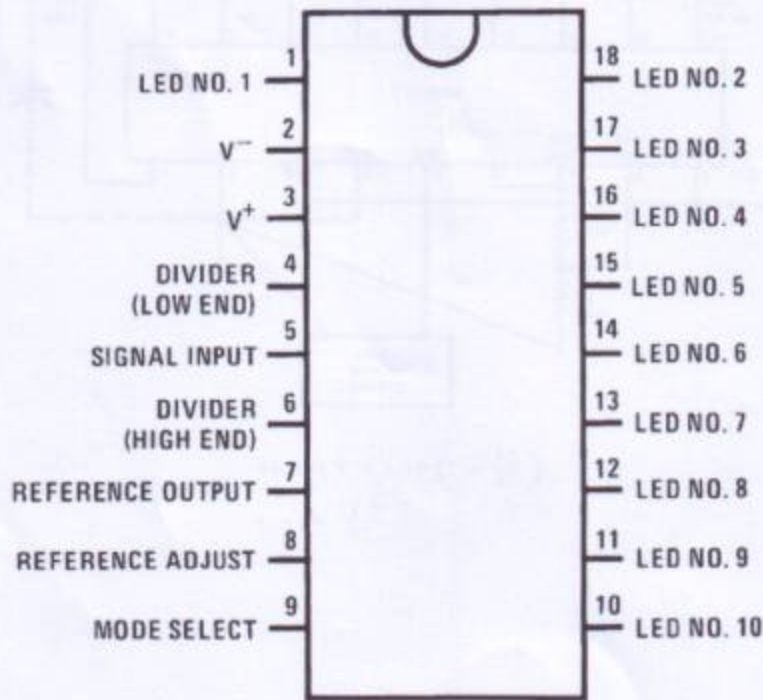

Top View


00707019

Working Principles

Here we use two pots. We used one pot to vary the voltage division and we used the other pot to vary the range of voltage.

Basic Bar Graph Meter :

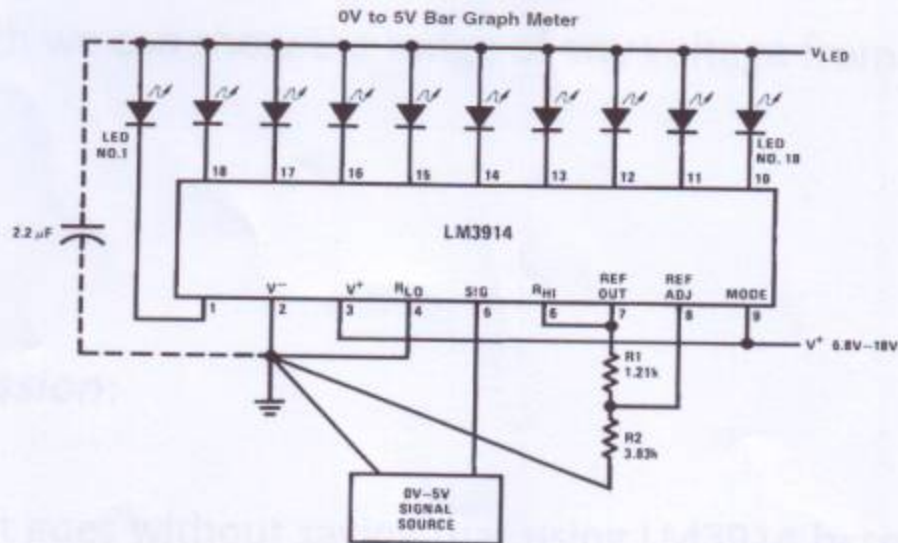We used the pin 4 for varying the division of voltage. The pin 5 is connected to pin 5 to control the range of voltage. We used pin 2 for grounding. We used the 5v to 12v as an example.



$$\text{Ref Out } V = 1.25 \left(1 + \frac{R_2}{R_1} \right)$$

$$I_{LED} \approx \frac{12.5}{R_1}$$

Working Principle:

Here we use two pots. We used one pot to vary the voltage division and we used the other pot to vary the range of voltage.

We used the pot connected to the pin 4 for varying the division of voltages. The pot connected to pin 5 to control the range of voltage. We used pin 2 for grounding. We used the 8v to 12v as for example.

Though we can show the range of any voltage from 4 to 22v.

Discussion:

Now, it goes without saying that using LM3914 based our device can monitor a battery very smoothly. We can observe the charge level of any kind of dc battery. This device is very essential for observe the level of charge of DC source.

10.01.05.072
10.01.05.077
10.01.05.080
10.01.05.084
10.01.05.104